


Analog Lab

WEEK -2 Experiment REPORT

Arpit Katiyar(24F1100064)

Objective :-


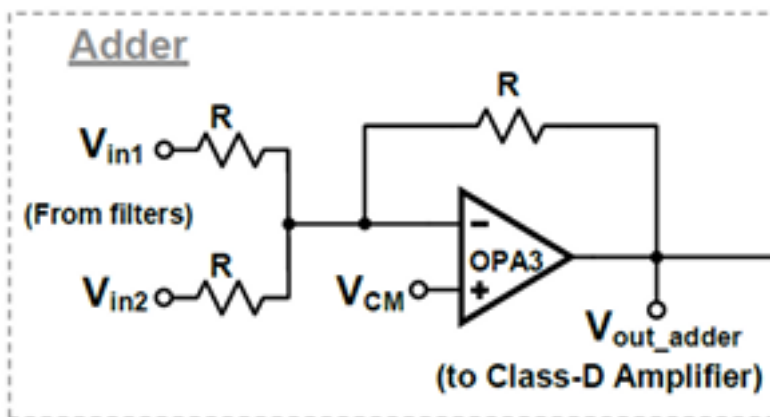
The objective of experiment-5 is to add the band pass filtered signals (V_{out_bpf1} and V_{out_bpf2}) from experiment-4. The schematic diagram of an adder is given below.




Required Material:-


1. MCP6004 as OPamps
2. Resistors
3. Power supply and Sinusoid wave (Adalm 1000)
4. Wire breadboard etc.

LT Spice Circuit And Output

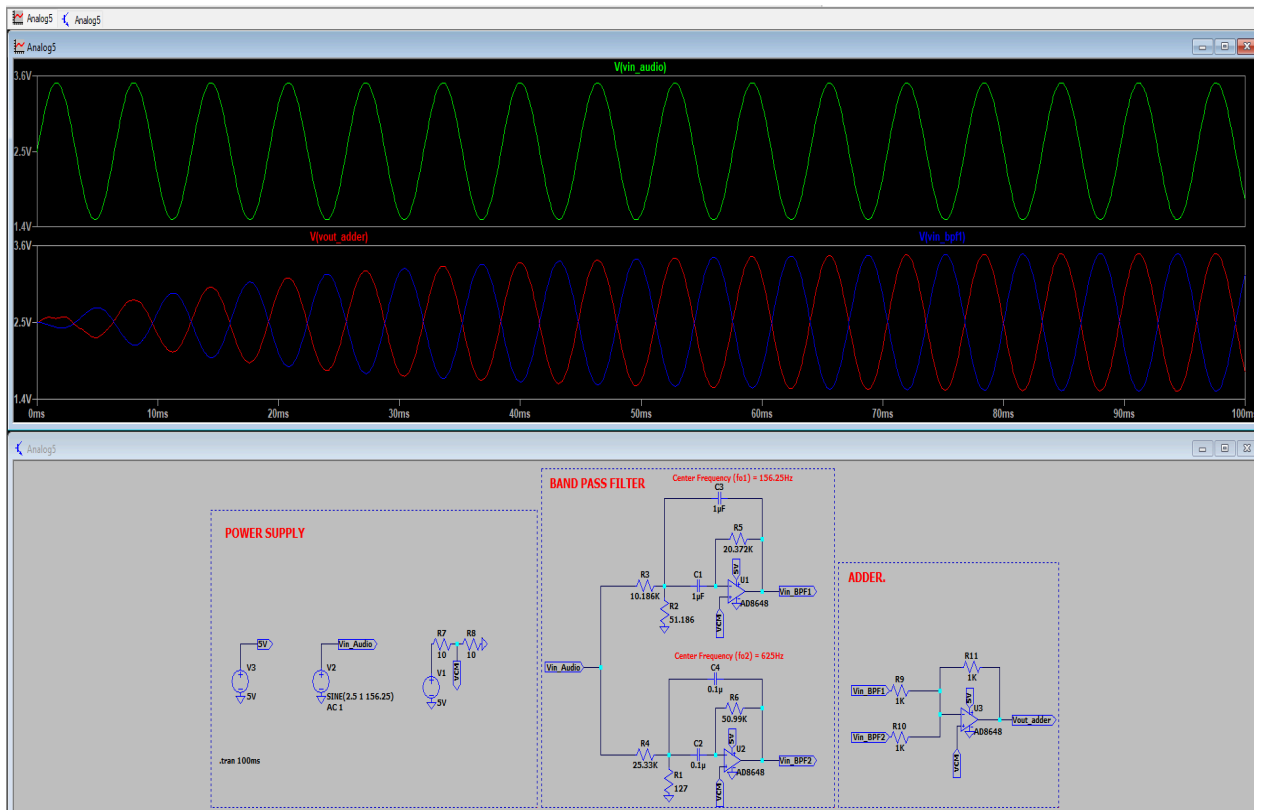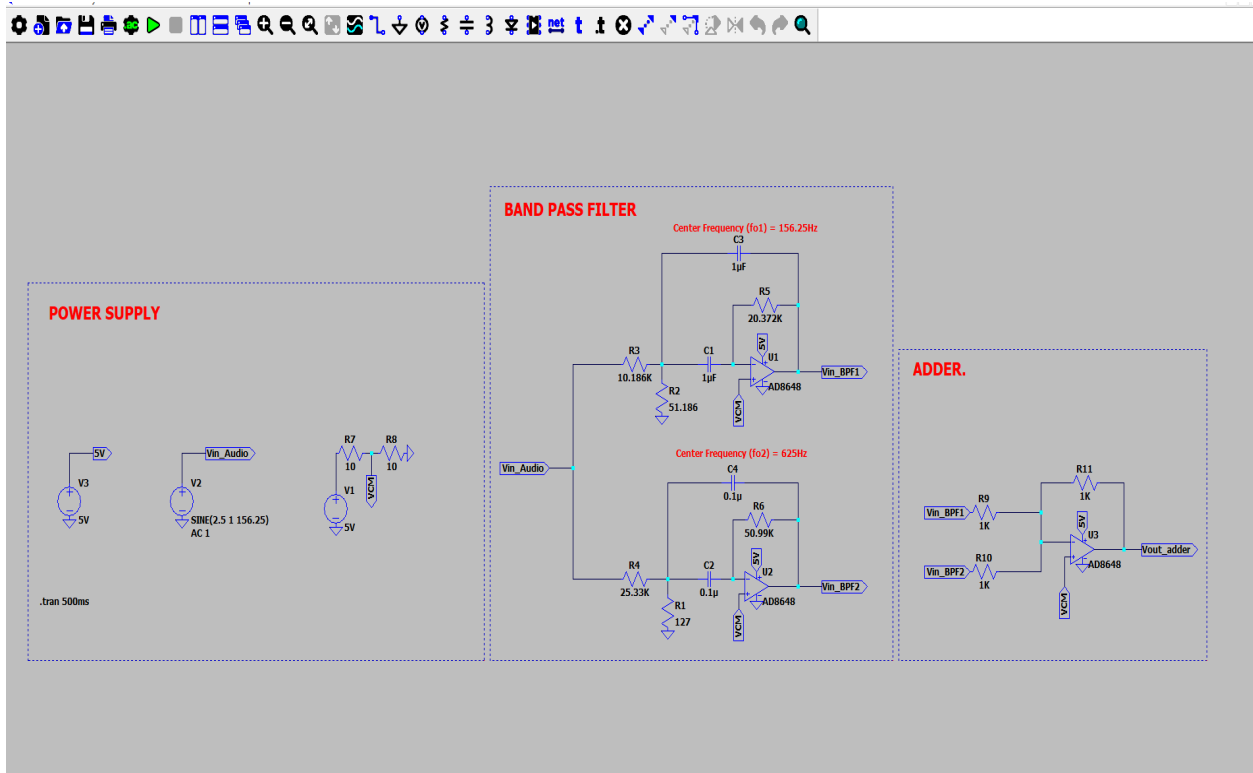

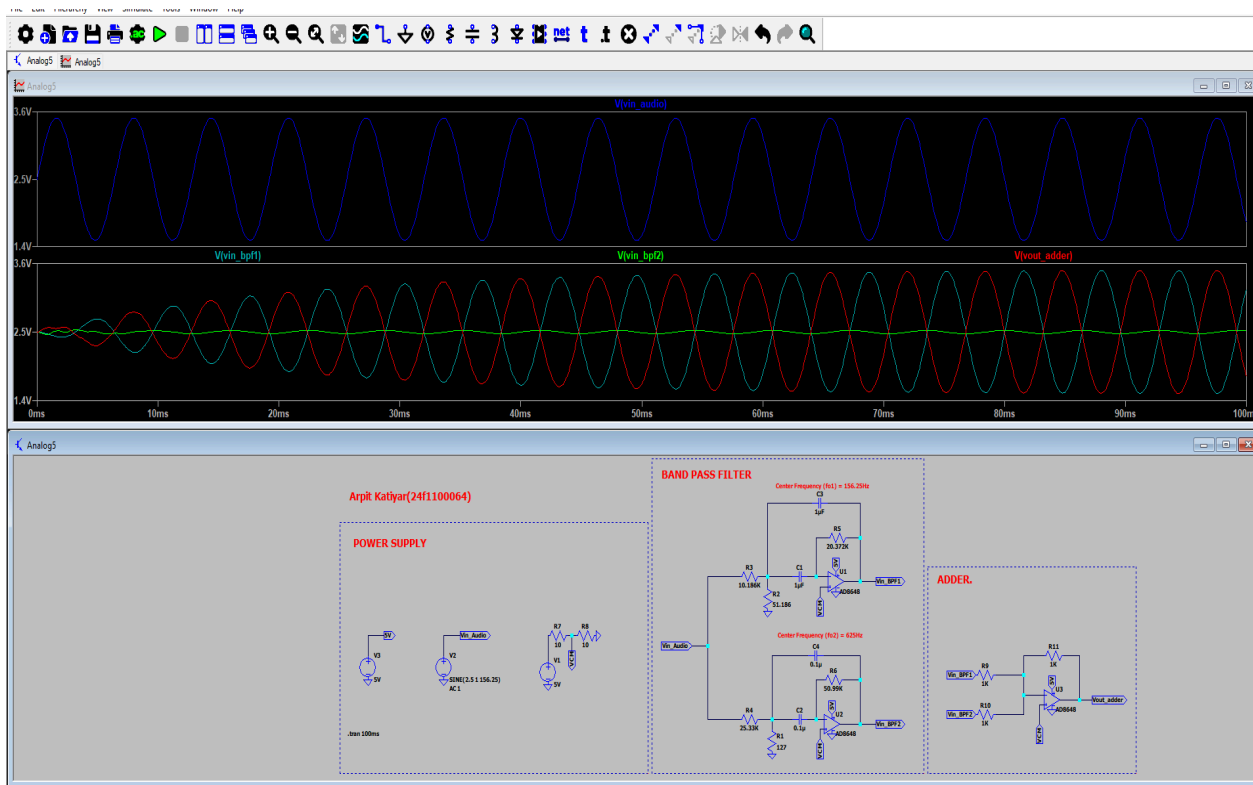

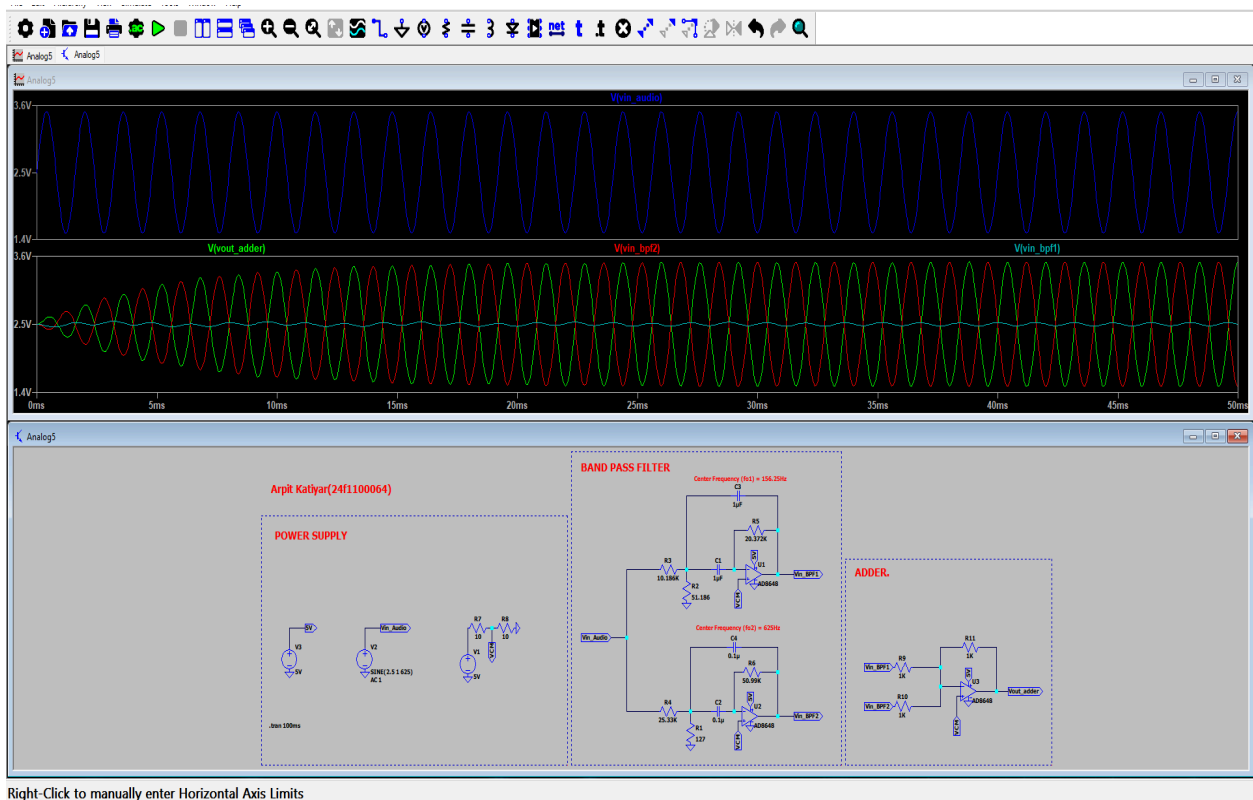Click to plot V(Vout_adder). DC operating point: V(Vout_adder) = 2.5006018V



Right-Click to manually enter Horizontal Axis Limits

